


## Modulo-4 Up-Down Counter

This is a counter with input.

If  $X = 0$ , the device counts up: 0, 1, 2, 3, 0, 1, 2, 3, etc.

If  $X = 1$ , the device counts down: 0, 3, 2, 1, 0, 3, 2, 1, etc.

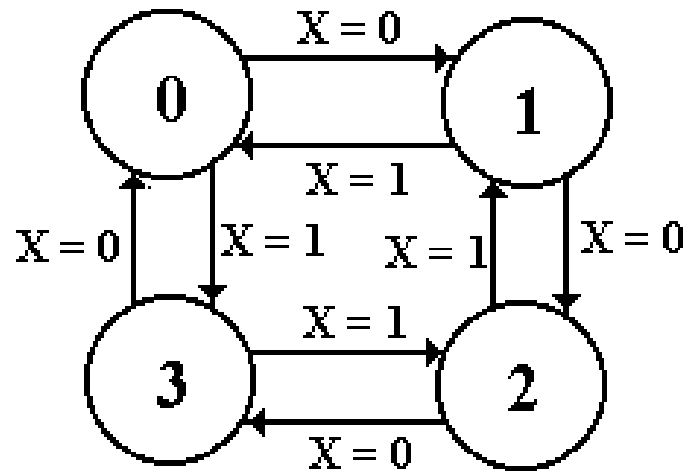**Step 1a: Derive the state diagram and state table for the circuit.**



Note two transitions between the state pairs: one is up and one is down.

## Step 1b: Derive the State Table

Present State	Next State	
	X = 0	X = 1
0	1	3
1	2	0
2	3	1
3	0	2

This is just a restatement of the state diagram.

Note: Two columns for the “Next State”.

## Step 2: Count the States and Determine the Flip–Flop Count

### Count the States

There are four states for any modulo–4 counter.  $N = 4$

The states are simple: 0, 1, 2, and 3.

### Calculate the Number of Flip–Flops Required

Let  $P$  be the number of flip–flops.

Solve  $2^{P-1} < N \leq 2^P$ .      So  $2^{P-1} < 4 \leq 2^P$  and  $P = 2$ .

We need two flip–flops.

### **Step 3: Assign a unique P-bit binary number (state vector) to each state.**

Here  $P = 2$ , so we are assigning two-bit binary numbers.

Vector is denoted by the binary number  $Y_1 Y_0$ .

State	2-bit Vector
	$Y_1 Y_0$
0	0 0
1	0 1
2	1 0
3	1 1

Each state has a unique 2-bit number assigned.

Any other assignment would be absurd.

## Step 4: Derive the state transition table and the output table.

There is no computed output, hence no output table.

The state transition table uses the 2-bit state vectors

Present State		Next State	
		X = 0	X = 1
0	00	01	11
1	01	10	00
2	10	11	01
3	11	00	10

## Step 5: Separate the state transition table into P tables, one for each flip-flop.

### Flip-Flop 1

Flip-Flop 1		
PS	Next State: $Y_1$	
$Y_1 Y_0$	$X = 0$	$X = 1$
0 0	0	1
0 1	1	0
1 0	1	0
1 1	0	1

### Flip-Flop 0

Flip-Flop 0: $Y_0$		
PS	Next State	
$Y_1 Y_0$	$X = 0$	$X = 1$
0 0	1	1
0 1	0	0
1 0	1	1
1 1	0	0

**Step 6: Decide on the types of flip-flops to use.  
When in doubt, use all JK's.**

Here is the excitation table for a JK flip-flop

Q(T)	Q(T+1)	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

## Step 7: Derive the input table for each flip-flop

### Flip-Flop 1

	X = 0			X = 1		
$Y_1 Y_0$	$Y_1$	$J_1$	$K_1$	$Y_1$	$J_1$	$K_1$
<b>0</b> 0	<b>0</b>	0	d	<b>1</b>	1	d
<b>0</b> 1	<b>1</b>	1	d	<b>0</b>	0	d
<b>1</b> 0	<b>1</b>	d	0	<b>0</b>	d	1
<b>1</b> 1	<b>0</b>	d	1	<b>1</b>	d	0

### Flip-Flop 0

	X = 0			X = 1		
$Y_1 Y_0$	$Y_0$	$J_0$	$K_0$	$Y_1$	$J_0$	$K_0$
0 <b>0</b>	<b>1</b>	1	d	<b>1</b>	1	d
0 <b>1</b>	<b>0</b>	d	1	<b>0</b>	d	1
1 <b>0</b>	<b>1</b>	1	d	<b>1</b>	1	d
1 <b>1</b>	<b>0</b>	d	1	<b>0</b>	d	1

**Question:** How do we produce equations for the J's and K's?



## Step 8: Derive the input equations for each flip-flop

The equations are based on the present state and the input.

The input  $X$  produces a complication.

The simplest match procedure will lead to two equations for each flip-flop input: one for  $X = 0$  and one for  $X = 1$ .

Use the “combine rule”

The rule for combining expressions derived separately for  $X = 0$  and  $X = 1$  is

$$\bar{X} \bullet (\text{expression for } X=0) + X \bullet (\text{expression for } X=1).$$

Rationale: Let  $F(X) = A \bullet \bar{X} + B \bullet X$

When  $X = 0$ ,  $F(X) = A$  and when  $X = 1$ ,  $F(X) = B$ .

## Input Equations for Flip-Flop 1

	X = 0			X = 1		
<b>Y<sub>1</sub></b> Y <sub>0</sub>	<b>Y<sub>1</sub></b>	J <sub>1</sub>	K <sub>1</sub>	<b>Y<sub>1</sub></b>	J <sub>1</sub>	K <sub>1</sub>
<b>0</b> 0	<b>0</b>	0	d	<b>1</b>	1	d
<b>0</b> 1	<b>1</b>	1	d	<b>0</b>	0	d
<b>1</b> 0	<b>1</b>	d	0	<b>0</b>	d	1
<b>1</b> 1	<b>0</b>	d	1	<b>1</b>	d	0

$$J_1 = Y_0$$

$$K_1 = Y_0$$

$$J_1 = Y_0'$$

$$K_1 = Y_0'$$

Apply the “combine rule”

$$J_1 = X' \bullet Y_0 + X \bullet Y_0' = X \oplus Y_0$$

$$K_1 = X' \bullet Y_0 + X \bullet Y_0' = X \oplus Y_0$$

## Input Equations for Flip-Flop 0

	X = 0			X = 1		
$Y_1 Y_0$	$Y_0$	$J_0$	$K_0$	$Y_1$	$J_0$	$K_0$
0 0	1	1	d	1	1	d
0 1	0	d	1	0	d	1
1 0	1	1	d	1	1	d
1 1	0	d	1	0	d	1

$$J_0 = 1$$

$$K_0 = 1$$

$$J_0 = 1$$

$$K_0 = 1$$

Apply the “Combine Rule”

$$J_0 = X' \bullet 1 + X \bullet 1 = 1$$

$$K_0 = X' \bullet 1 + X \bullet 1 = 1$$

Neither  $J_0$  nor  $K_0$  depend on  $X$ . But  $Y_0$  does not depend on  $X$ .

## Step 9: Summarize the equations by writing them in one place.

Here they are.

$$J_1 = X \oplus Y_0$$


$$J_0 = 1$$

$$K_1 = X \oplus Y_0$$

$$K_0 = 1$$


## Step 10: Draw the Circuit

As designed, it is:

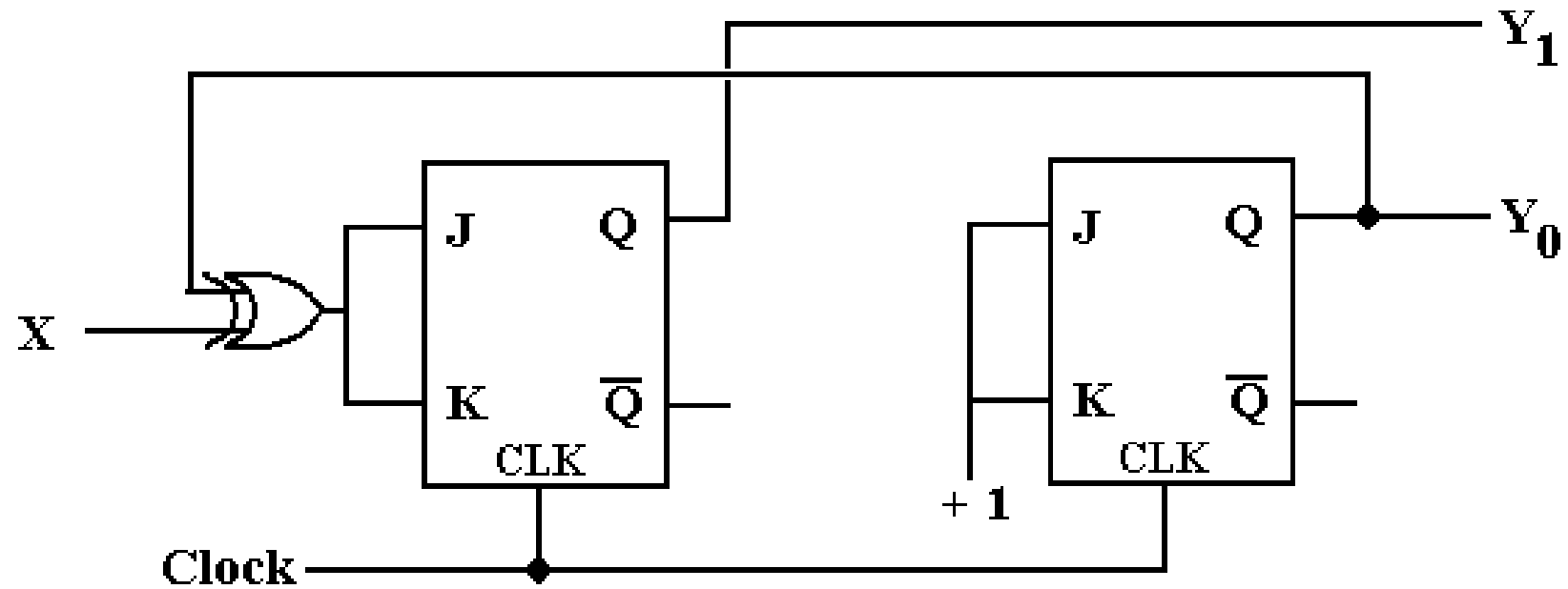

## Step 10: Draw the Circuit

Implemented with T Flip-Flops, it is:

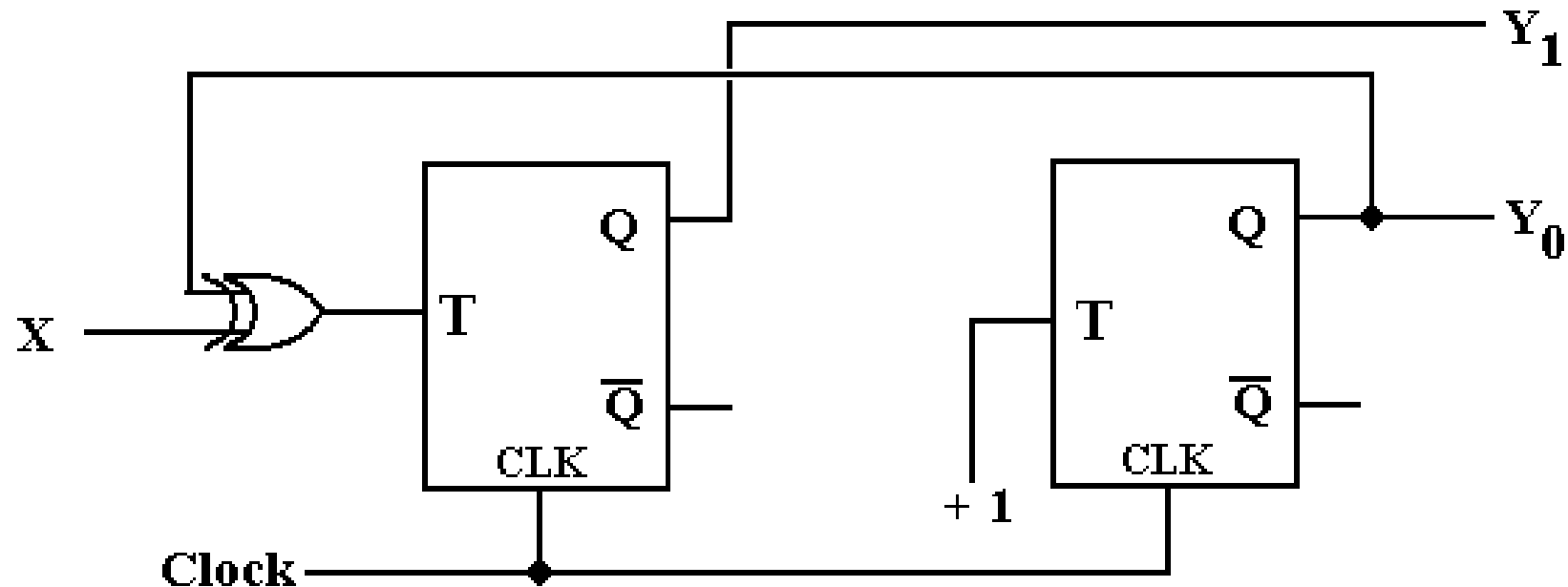

One could also use a 4-register “one hot” design, with the input  $X$  used to determine the direction of the shift.